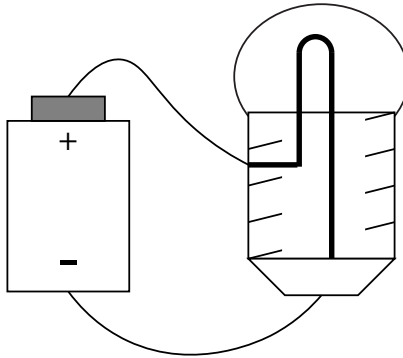


Lab 11: Current Electricity

3. Clearly mark the closed circuit.



4. Draw the arrangements that will light the bulb here.

5. Draw your circuit here.

6. Draw your circuit here.

7. Draw your flashlight circuit here.